

## High Frequency Electronics, 2018, Heikki Valmu

Done by Kun ZHU

The synthesizer at page 8 of the document HFele amps synths.pptx. :

1. Calculate the output frequency of the synthesizer if the reference frequency is 10 MHz, the multiplier of the frequency multiplier (M) is 10 and the prescaler values are:  $N_6=10$ ,  $N_5=2$ ,  $N_4=3$ ,  $N_3=10$ ,  $N_2=2$ ,  $N_1=10$ .

The prescaler values are digitally controlled. If you want to decrease the frequency by 1 MHz by changing one of the values, which prescaler value you have to increase or decrease by 1? What if you want to increase the value by 500 MHz?

$$f_o = \left[ M \left( \frac{N_6}{N_5} + \frac{N_4}{N_3} \right) + \frac{N_2}{N_1} \right] f_{ref} = \left[ 10 \times \left( \frac{10}{2} + \frac{3}{10} \right) + \frac{2}{10} \right] \times 10^7 = 532 \text{ MHz}$$

If

$$f_o = \left[ M \left( \frac{N_6}{N_5} + \frac{N_4}{N_3} \right) + \frac{N_2}{N_1} \right] f_{ref} = 531 \text{ MHz}$$

We should change  $N_2 = 1$

So,

$$f_o = \left[ M \left( \frac{N_6}{N_5} + \frac{N_4}{N_3} \right) + \frac{N_2}{N_1} \right] f_{ref} = \left[ 10 \times \left( \frac{10}{2} + \frac{3}{10} \right) + \frac{1}{10} \right] \times 10^7 = 531 \text{ MHz}$$

If

$$f_o = \left[ M \left( \frac{N_6}{N_5} + \frac{N_4}{N_3} \right) + \frac{N_2}{N_1} \right] f_{ref} = 32 \text{ MHz}$$

We should change  $N_6 = 20$

So,

$$f_o = \left[ M \left( \frac{N_6}{N_5} + \frac{N_4}{N_3} \right) + \frac{N_2}{N_1} \right] f_{ref} = \left[ 10 \times \left( \frac{20}{2} + \frac{3}{10} \right) + \frac{1}{10} \right] \times 10^7 \\ = 1.032 \text{ GHz}$$

2. Rename the multiplication factor of the frequency multiplier as  $M_2$  (previously M) and place as well a frequency multiplier with a multiplication factor of  $M_1$  before / below the previous mixer.

Redraw the circuit.

Derive an equation for its output frequency (as a function of  $f_{REF}$  and the factors  $N_i$  and  $M_i$ ).

Please find answer in page 2.

$$\frac{f_{ref}}{N_5} = \frac{f_2}{N_6} \rightarrow f_2 = \frac{N_6}{N_5} f_{ref}$$

$$\frac{f_{ref}}{N_3} = \frac{f_1 - M_1 f_2}{N_4} \rightarrow f_1 = \left( \frac{N_4}{N_3} + M_1 \cdot \frac{N_6}{N_5} \right) f_{ref}$$

$$\frac{f_{ref}}{N_1} = \frac{f_0 - M_2 f_1}{N_2} \rightarrow f_0 = \left( \frac{N_2}{N_1} + M_2 \left( \frac{N_4}{N_3} + M_1 \cdot \frac{N_6}{N_5} \right) \right) f_{ref}$$

